



**FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND COMPUTER
ENGINEERING**

ENEE4403

POWER SYSTEMS

project

Prepared by:

Karim taha 1211155

Supervised by:

Dr.Jaser Sa'Ed

January , 15, 2025

Abstract

This project aims to take knowledge about power simulator this program is used to implement high voltage systems it shows all the necessary data (transmission impedance, bus voltage, power losses, and the Y bus matrix) it helps to analyze the circuit and see the fault currents and voltage impacts and detect the condition of the system when the load is changed

Contents

Abstract	i
Production	1
connection.....	1
Question1	3
Question 2-part a	6
Question 2-part b	7
Question 2-part c.....	7
Question 2 -part d	8
Question 2-part e.....	8
Question 3 Fully loaded Transformer	9
Question 4 shunt capacitor	11
Question 5 Fault.....	15
Conclusion.....	18

Table of Figures

Figure 1:bus option	1
Figure 2:generator settings	1
Figure 3:transformer setting.....	2
Figure 4: power word parameter calculator	3
Figure 5:L1 parameter	4
Figure 6:L3 parameter	4
Figure 7:L2 parameter	4
Figure 8:L5 parameter	4
Figure 9:L4 parameter	4
Figure 10:system as the required data.....	5
Figure 11:system structure	6
Figure 12:running the system.....	6
Figure 13:Total load, power and losses	7
Figure 14: System before increasing the load	9
Figure 15:system when the transformer T1 overloaded.....	9
Figure 16: the value of the load on Bus 3 when T1 is fully loaded.....	10
Figure 17:before the capacitor	11
Figure 18: after adding the capacitor	11
Figure 19:total load generator and loses when shunt =35Mvar.....	12
Figure 20:after increase the value of the capacitor to51Mvar.....	12
Figure 21:total load generator and loses when the shunt =51MVR	13
Figure 22:System with shunt =28Mvar	13
Figure 23:total load when shunt =28Mvar	14
Figure 24::Transmission 3 line fault parameter.....	15
Figure 25:Transmission 5 line fault parameter.....	15
Figure 26:Transmission 4 line fault parameter.....	15
Figure 27:Transmission 2 line fault parameter.....	15
Figure 28:Transmission 1 line fault parameter.....	15
Figure 29: fault at bus4	15
Figure 30: lines recoded	17

List of Table

Table 1:Transmtion line parameters Table.....	4
Table 2:Y Bus Matrix	7
Table 3:Busess data	8
Table 4:Branches state	8

Production

System Connection

the bus setting of the slack bus where the bus can be added by inserting the bus from the draw and fill the required information from name, nominal voltage and fill the required information from name, nominal voltage

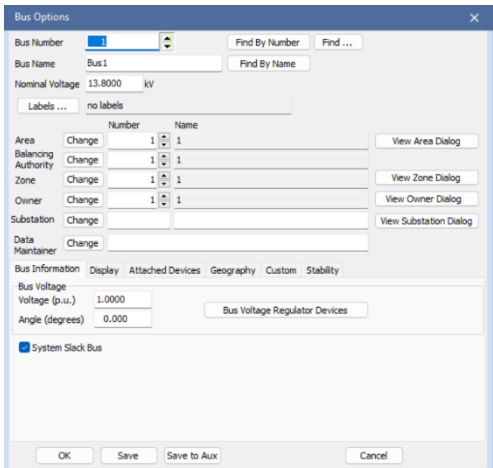


Figure 1:bus option

The generator can be implemented by using the draw option and the required data must be added

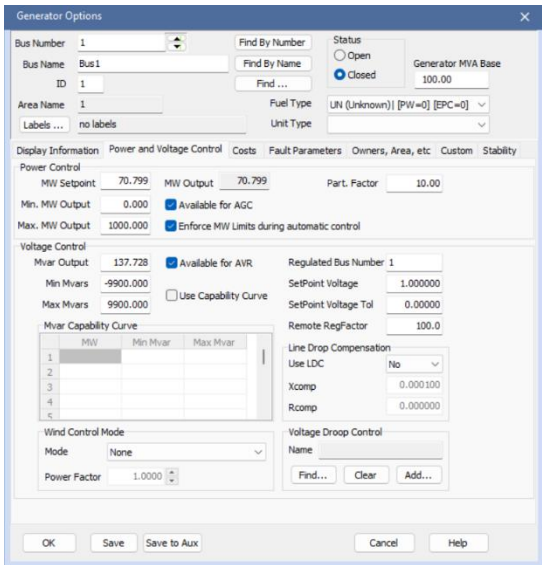


Figure 2:generator settings

The transformer setting

The screenshot shows the 'Branch Options' dialog box with the 'Transformer' tab selected. The 'From Bus' is set to '2' (BUS 2) and the 'To Bus' is set to '1' (Bus1). The 'Circuit' is set to '1'. The 'Nominal kV' for the 'From Bus' is 230.0 and for the 'To Bus' is 13.80. The 'Status' is set to 'Closed'. The 'Branch Device Type' is set to 'Transformer'. The 'Length' is set to 0.00. The 'Calculate Impedances' button is visible. The 'Normal Status' is set to 'Closed'. The 'D-FACTS Devices on the Line' checkbox is unchecked. The 'Has D-FACTS' checkbox is unchecked. The 'MVA Limits' table is shown on the right.

MVA Limits	Limit A	Limit B	Limit C	Limit D	Limit E	Limit F	Limit G	Limit H	Limit I	Limit J	Limit K
Limit A	200.000										
Limit B		0.000									
Limit C			0.000								
Limit D				0.000							
Limit E					0.000						
Limit F						0.000					
Limit G							0.000				
Limit H								0.000			
Limit I									0.000		
Limit J										0.000	
Limit K											0.000

Figure 3:transformer setting

Question1: calculate per unit impedances for all transmission lines

calculating per-unit impedances

the base impedance was calculated to find the value of pre-unit impedance manually and it can be done without calculating using the per unit calculator in the power word simulator when the line be added

$$Z_{PU} = \frac{Z_{actual}}{Z_{base}}, Y_{PU} = \frac{Y_{actual}}{Y_{base}}$$

$$Z_{base} = \frac{V_{rated}^2}{S_{base}} = \frac{230^2}{100} = 529$$

$$Y_{base} = \frac{1}{Z_{base}} = 1.890 \times 10^{-3}$$

the calculator impedance of the power word simulator was used to calculate the parameter of the transmission line in the up

Line Per Unit Impedance Calculator

Actual Impedance and Current Limits

R (Ohms/km) 0.080000
X (Ohms/km) 0.500000
B (Mhos/km) 3.3 x 10⁻⁶
G (Mhos/km) -0.000015 x 10⁻⁶

Limit A (Amps) 1004.087
Limit B (Amps) 0.000
Limit C (Amps) 0.000
Limit D (Amps) 0.000
Limit E (Amps) 0.000
Limit F (Amps) 0.000
Limit G (Amps) 0.000
Limit H (Amps) 0.000
Limit I (Amps) 0.000
Limit J (Amps) 0.000
Limit K (Amps) 0.000
Limit L (Amps) 0.000
Limit M (Amps) 0.000
Limit N (Amps) 0.000

Line Length

15.000 km
When changing convert:
☒ PU/MVA <-->
☐ <--- Electrical

Length Units

☐ miles
☒ kilometers

System Base Values

Power Base (MVA) 100.0000
Voltage Base (kV) 230.000
Impedance Base (Ohms) 529.000
Admittance Base (Mhos) 0.00189036

Per Unit Impedance and MVA Limits

R (pu) 0.002268
X (pu) 0.014177
B (pu) 0.026186
G (pu) 0.000000

Limit A (MVA) 400.000
Limit B (MVA) 0.000
Limit C (MVA) 0.000
Limit D (MVA) 0.000
Limit E (MVA) 0.000
Limit F (MVA) 0.000
Limit G (MVA) 0.000
Limit H (MVA) 0.000
Limit I (MVA) 0.000
Limit J (MVA) 0.000
Limit K (MVA) 0.000
Limit L (MVA) 0.000
Limit M (MVA) 0.000
Limit N (MVA) 0.000

OK Help Cancel

Figure 4: power word parameter calculator

lines parameter

The per-unit impedance of the L2 was calculated manually as shown below:

$$Z_{pu} = \frac{Z_{Actual}}{Z_{base}} = \left(\frac{0.08 + j0.5}{529} \right) * 28 = 0.04233 + j0.026459$$

The values of the line parameter of each line are shown in the figure below:

Figure 5:L1 parameter

Figure 7:L2 parameter

Figure 6:L3 parameter

Figure 9:L4 parameter

Figure 8:L5 parameter

The parameters of each line are shown in the table below this table can be found in case >>>> branch input the value of each parameter depends on length of each line

Table 1:Transmtion line parameters Table

	To Number	To Name ▲	Circuit	Status	Branch Device Type	Xfrmr	R	X	B	Lim MVA A
1	3	Bus 3	1	Closed	Line	NO	0.00423	0.02646	0.04888	400.0
2	3	Bus 3	1	Closed	Line	NO	0.00227	0.01418	0.02619	400.0
3	1	Bus1	1	Closed	Transformer	YES	0.00000	0.10000	0.00000	200.0
4	5	Bus5	1	Closed	Line	NO	0.00227	0.01418	0.02619	400.0
5	5	Bus5	1	Closed	Line	NO	0.00604	0.03779	0.06984	400.0
6	6	Bus6	1	Closed	Line	NO	0.00755	0.04723	0.08732	400.0
7	7	Bus7	1	Closed	Transformer	YES	0.00000	0.10000	0.00000	200.0

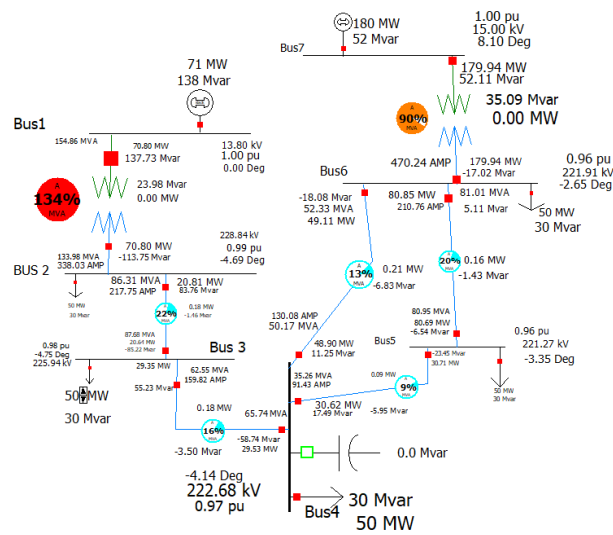


Figure 10: system as the required data

As noted transformer one is fully loaded since the total loaded power is 250 MW and 150 MVar and the generation power is equal to 250.8 MW and 189MVar so this surplus will affect the complex power that is on the slack bus is higher than the rated value on the transformer so the transformer will be full loaded so the value of the complex power of the transformer was changed to 200MVar

Question 2-part a

One-line diagram with data

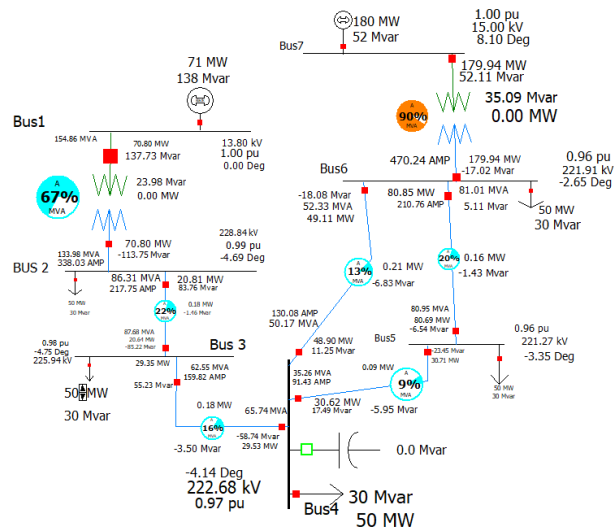


Figure 11: system structure

running the system

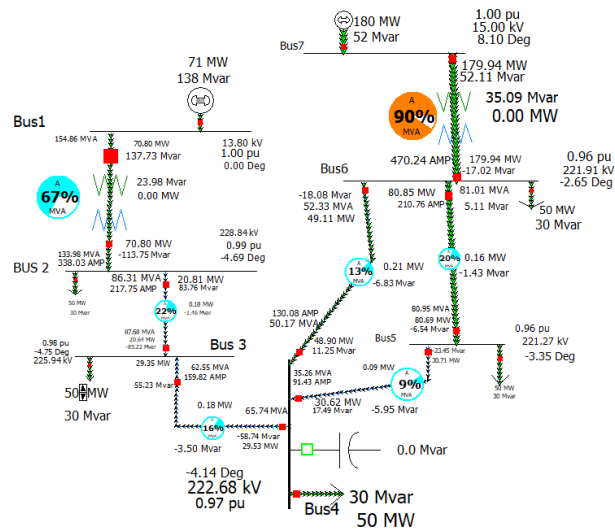


Figure 12: running the

Question 2-part b

Total load, total generation power, and total losses this data can be seen from the case summary:

Case Summary for Present

Number of Devices in Case			
Buses	7	Trans. Lines (AC)	5
Generators	2	Series Capacitors	0
Loads	5	LTCs (Control Volt)	0
Switched Shunts	0	Phase Shifters	0
2 Term. DC Lines	0	Mvar Controlling	0
Multi-Term. DC	0		
Breakers	0	Fuses	0
Disconnects	0	Load Break Disc.	0
ZBRs	0	Ground Disconnects	0
Areas	1	Islands	1
Zones	1	Interfaces	0
Substations	0	Injection Groups	0

Case pathname: C:\Users\97059\project_22222.PWB

Case Totals (for in-service devices only)		
	MW	Mvar
Load	250.0	150.0
Generation	250.8	189.9
Shunts	0.0	0.0
Losses	0.8	39.9
Dist Gen	0.0	0.0

Generator Spinning Reserves		
	Positive [MW]	Negative [MW]
	1749.2	250.8

Negative MW Loads and Generators		
	MW	Mvar
Load	0.0	0.0
Generation	0.0	0.0

Slack Buses:
Bus1 (1); in Area 1 (1)

Buttons: Print, Help, Close

Figure 13: Total load, power and losses

Question 2-part c

The y bus matrix can be found from the solution detail (Y bus matrix)

the table of Y bus matrix can be found from >>>solution detail >>> Y bus matrix

Table 2: Y Bus Matrix

	Number	Name	Bus 1	Bus 2	Bus 3	Bus 4	Bus 5	Bus 6	Bus 7
1	1	Bus1	9.00 - j10.00	-0.00 + j8.70					
2	2	BUS 2	-0.00 + j8.70	11.00 - j76.32	-11.00 + j68.78				
3	3	Bus 3		-11.00 + j68.78	16.90 - j105.59	-5.90 + j36.85			
4	4	Bus4			-5.90 + j36.85	13.32 - j83.20	-4.13 + j25.80	-3.30 + j20.65	
5	5	Bus5				-4.13 + j25.80	15.13 - j94.53	-11.00 + j68.78	
6	6	Bus6				-3.30 + j20.65	-11.00 + j68.78	14.30 - j99.37	-0.00 + j10.00
7	7	Bus7						-0.00 + j10.00	0.00 - j10.00

Question 2 -part d

Table 3:Busess data

	Number	Name	Area Name	Nom kV	PU Volt	Volt (kV)	Angle (Deg)	Load MW	Load Mvar	Gen MW	Gen Mvar	Switched Shunts Mvar	Act G Shunt MW	Act B Shunt Mvar	Area Num	Zone Num
1	1	Bus1	1	13.80	1.00000	13.800	0.00			70.82	137.77		0.00	0.00	1	1
2	2	Bus2	1	230.00	0.99490	228.827	-4.70	50.00	30.00				0.00	0.00	1	1
3	3	Bus3	1	230.00	0.98230	225.930	-4.76	50.00	30.00				0.00	0.00	1	1
4	4	Bus4	1	230.00	0.96811	222.666	-4.14	50.00	30.00				0.00	0.00	1	1
5	5	Bus5	1	230.00	0.96201	221.262	-3.35	50.00	30.00				0.00	0.00	1	1
6	6	Bus6	1	230.00	0.96477	221.897	-2.65	50.00	30.00				0.00	0.00	1	1
7	7	Bus7	1	15.00	1.00000	15.000	8.10			180.00	52.17		0.00	0.00	1	1

Question 2-part e

Table 4:Branches state

Branches State																
X Buses X DC Lines X Branches Input X Ybus																
Records Geo Set Columns Find... Remove Quick Filter																
Filter Advanced Branch																
	From Number	From Name	To Number	To Name	Circuit	Status	Branch Device Type	Xfmr	MW From	Mvar From	MVA From	Lim MVA	% of MVA Limit (Max)	MW Loss	Mvar Loss	
1	2	BUS 2	1	Bus1	1	Closed	Transforme	YES	-70.8	-113.8	134.0	200.0	77.5	0.00	24.00	
2	2	BUS 2	3	Bus 3	1	Closed	Line	NO	20.8	83.8	86.3	400.0	21.9	0.18	-1.46	
3	4	Bus4	3	Bus 3	1	Closed	Line	NO	29.5	-58.7	65.7	400.0	16.4	0.18	-3.50	
4	4	Bus4	5	Bus5	1	Closed	Line	NO	-30.6	17.5	35.3	400.0	9.7	0.09	-5.95	
5	4	Bus4	6	Bus6	1	Closed	Line	NO	-48.9	11.2	50.2	400.0	13.1	0.21	-6.83	
6	6	Bus6	5	Bus5	1	Closed	Line	NO	80.9	5.1	81.0	400.0	20.3	0.16	-1.43	
7	6	Bus6	7	Bus7	1	Closed	Transforme	YES	-180.0	-17.0	180.8	200.0	93.7	0.00	35.12	

This table shows the apparent power (real power +j reactive power) that has been dissipated in the transmission line and passes through the transformers and the limit of MVA the reactive power losses much higher than the real power since the long distance of the transmission line and the high current that pass through the transmission line.

The direction of the power value is determined by the power angle, transitioning from a higher power angle to a lower one. The current value in a transmission line varies due to differences in line length, with Z_{pu} being influenced by this length. Moreover, an increase in the transmission line's length leads to greater losses, as Z rises in proportion to the length, resulting in a reduction of current within the line. The power in the line is influenced by the power angle, with power flow remaining stable for $\delta < 90^\circ$ and becoming unstable for $\delta > 90^\circ$. This simulation offers the voltage and angle for each bus, in addition to the quantity of power (both real power in MW and reactive power in MVar) utilized at every bus. It likewise illustrates how much power is lost within the system, both real and reactive, as well as the current that flows through the transmission lines and transformers.

Question 3 Fully loaded Transformer

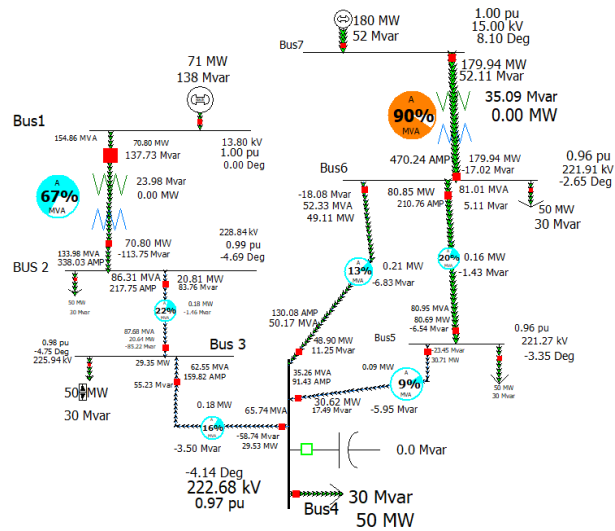


Figure 14: System before increasing the load


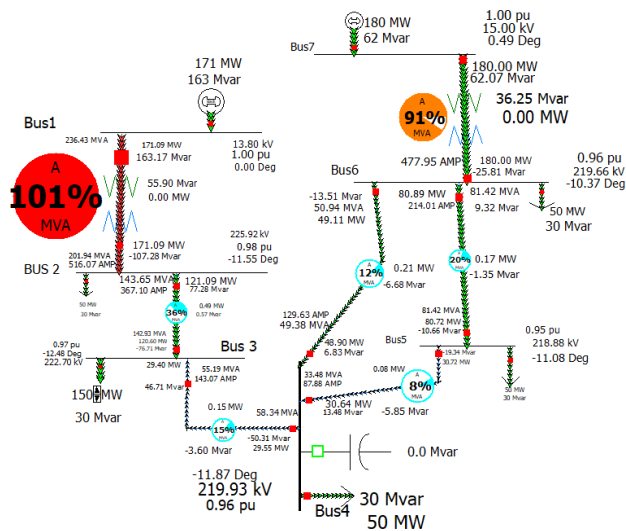



Figure 15: system when the transformer T1 overloaded

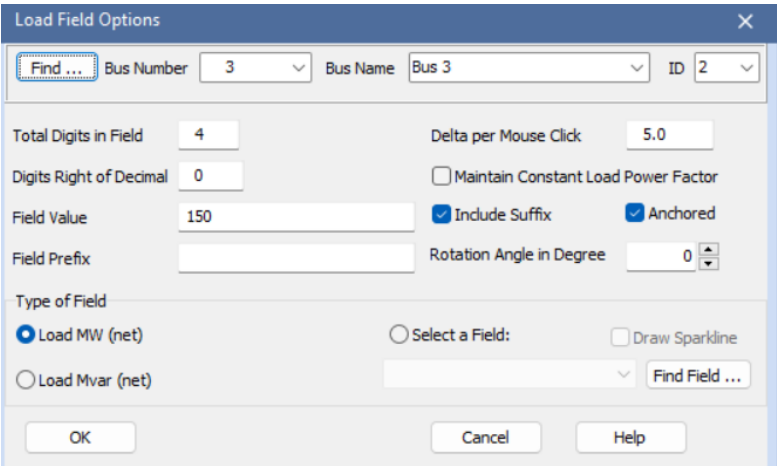The value that makes the T1 fully loaded is 150MW



The 'Load Field Options' dialog box is shown. It contains fields for 'Find ...', 'Bus Number' (3), 'Bus Name' (Bus 3), and 'ID' (2). Below these are settings for 'Total Digits in Field' (4), 'Delta per Mouse Click' (5.0), 'Digits Right of Decimal' (0), 'Field Value' (150), 'Field Prefix', 'Rotation Angle in Degree' (0), 'Type of Field' (Load MW (net) selected), 'Include Suffix' (checked), 'Anchored' (checked), 'Maintain Constant Load Power Factor' (unchecked), 'Select a Field' (empty), 'Draw Sparkline' (unchecked), and 'Find Field ...'. At the bottom are 'OK', 'Cancel', and 'Help' buttons.

Figure 16: the value of the load on Bus 3 when T1 is fully loaded

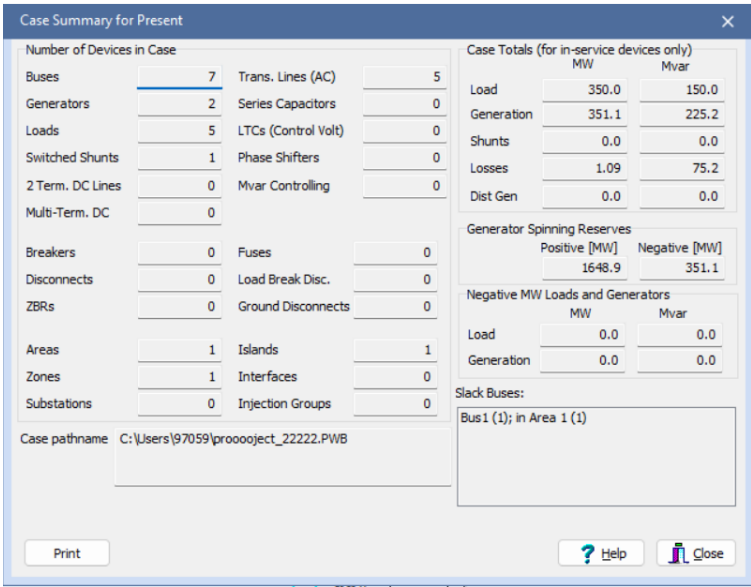

The 'Case Summary for Present' dialog box displays a summary of the current case. It includes a table of 'Number of Devices in Case' and a table of 'Case Totals (for in-service devices only)'. The 'Case Totals' table shows Load (350.0 MW, 150.0 Mvar), Generation (351.1 MW, 225.2 Mvar), Shunts (0.0 MW, 0.0 Mvar), Losses (1.09 MW, 75.2 Mvar), and Dist Gen (0.0 MW, 0.0 Mvar). The 'Generator Spinning Reserves' table shows Positive [MW] (1648.9) and Negative [MW] (351.1). The 'Negative MW Loads and Generators' table shows Load (0.0 MW, 0.0 Mvar) and Generation (0.0 MW, 0.0 Mvar). The 'Slack Buses' section lists Bus 1 (1) in Area 1 (1). The 'Case pathname' is C:\Users\97059\project_22222.PWB. At the bottom are 'Print', 'Help', and 'Close' buttons.

Number of Devices in Case			
Buses	7	Trans. Lines (AC)	5
Generators	2	Series Capacitors	0
Loads	5	LTCs (Control Volt)	0
Switched Shunts	1	Phase Shifters	0
2 Term. DC Lines	0	Mvar Controlling	0
Multi-Term. DC	0		
Breakers	0	Fuses	0
Disconnects	0	Load Break Disc.	0
ZBRs	0	Ground Disconnects	0
Areas	1	Islands	1
Zones	1	Interfaces	0
Substations	0	Injection Groups	0

Case Totals (for in-service devices only)			
	MW	Mvar	
Load	350.0	150.0	
Generation	351.1	225.2	
Shunts	0.0	0.0	
Losses	1.09	75.2	
Dist Gen	0.0	0.0	

Generator Spinning Reserves			
	Positive [MW]	Negative [MW]	
	1648.9	351.1	

Negative MW Loads and Generators			
	MW	Mvar	
Load	0.0	0.0	
Generation	0.0	0.0	

Slack Buses:
Bus 1 (1); in Area 1 (1)

Figure 17:power generator and losses at full loaded

The losses of the transmission line increased since the current in the transmission increased which directly affects the losses ($P=I^2R$) when the load at Bus 3 rises to 150 MW, the voltage at Bus 3 along with other buses drops due to the increased current. Transmission lines and transformers near Bus 3 can handle more load, increasing power losses and the risk of overload. Generators must supply additional power, which may strain the system without a reactive power supply, voltage stability may be compromised. as losses increase, overall system efficiency decreases

Question 4 shunt capacitor

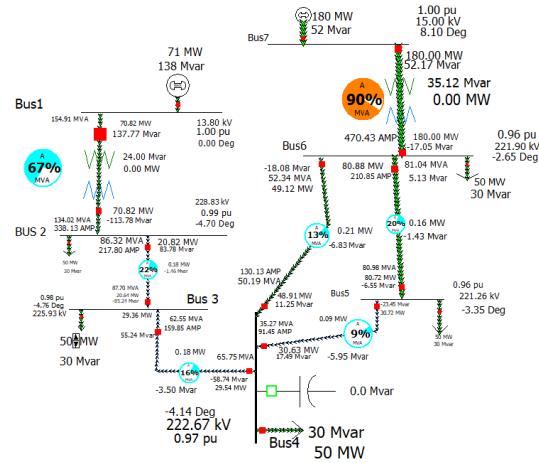


Figure 18: before the capacitor

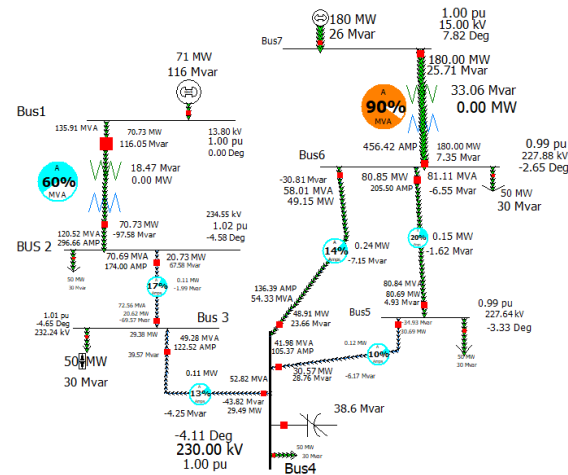


Figure 19: after adding the capacitor

$$C = \frac{Qc}{V^2w} = \frac{38.6 \times 10^6}{(230k)^2 (2 \times \pi \times 50)} = 2.323 \mu F$$

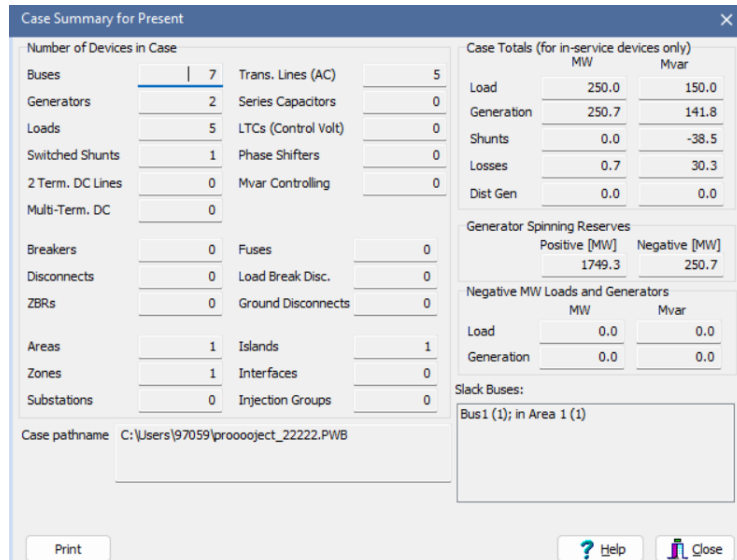


Figure 20: total load generator and losses when shunt = 38.6Mvar

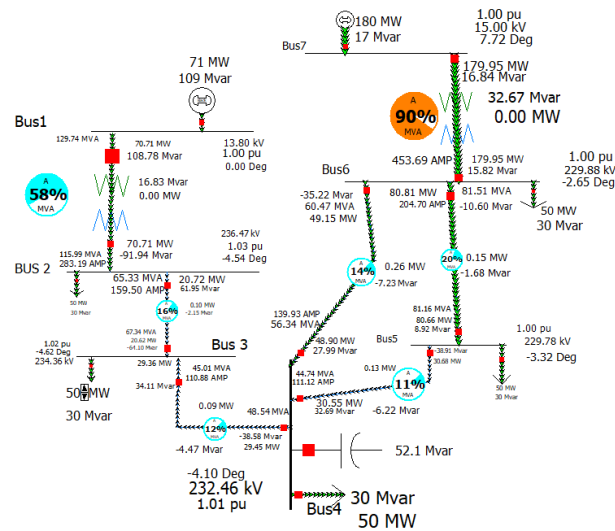


Figure 21: after increase the value of the capacitor to 51Mvar

$$C = \frac{Q_c}{V^2 \omega} = \frac{52.1 \times 10^6}{(230k)^2 (2\pi \times 50)} = 3.13 \mu F$$

Case Summary for Present					
Number of Devices in Case					
Buses	7	Trans. Lines (AC)	5	Case Totals (for in-service devices only)	
Generators	2	Series Capacitors	0	Load	250.0 MW 150.0 Mvar
Loads	5	LTCs (Control Volt)	0	Generation	250.7 MW 127.0 Mvar
Switched Shunts	1	Phase Shifters	0	Shunts	0.0 MW -50.9 Mvar
2 Term. DC Lines	0	Mvar Controlling	0	Losses	0.7 MW 27.9 Mvar
Multi-Term. DC	0			Dist Gen	0.0 MW 0.0 Mvar
Breakers	0	Fuses	0	Generator Spinning Reserves	
Disconnects	0	Load Break Disc.	0	Positive [MW]	1749.3
ZBRs	0	Ground Disconnects	0	Negative [MW]	250.7
Areas	1	Islands	1	Negative MW Loads and Generators	
Zones	1	Interfaces	0	Load	0.0 MW 0.0 Mvar
Substations	0	Injection Groups	0	Generation	0.0 MW 0.0 Mvar
Case pathname: C:\Users\97059\prooject_22222.PWB					
Slack Buses:					
Bus 1 (1); in Area 1 (1)					
Print ? Help Close					

Figure 22:total load generator and loses when the shunt =51MVR

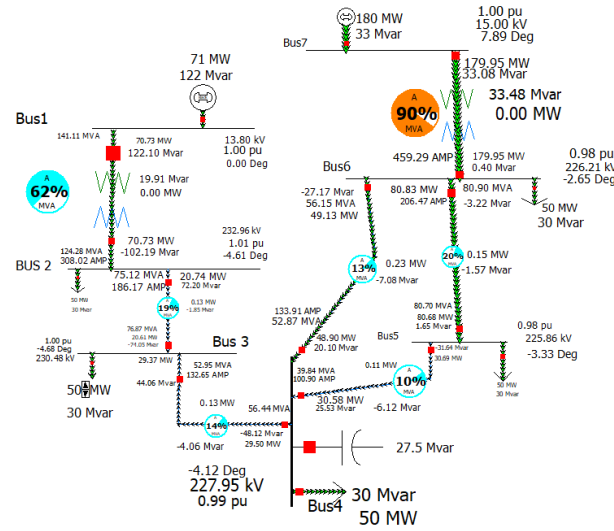


Figure 23:System with shunt =28Mvar

$$C = \frac{Q_c}{V^2 \omega} = \frac{27.5 \times 10^6}{(230k)^2 (2\pi \times 50)} = 1.6 \mu F$$

Case Summary for Present			
Number of Devices in Case			
Buses	7	Trans. Lines (AC)	5
Generators	2	Series Capacitors	0
Loads	5	LTCs (Control Volt)	0
Switched Shunts	1	Phase Shifters	0
2 Term. DC Lines	0	Mvar Controlling	0
Multi-Term. DC	0		
Breakers	0	Fuses	0
Disconnects	0	Load Break Disc.	0
ZBRs	0	Ground Disconnects	0
Areas	1	Islands	1
Zones	1	Interfaces	0
Substations	0	Injection Groups	0
Case pathname: C:\Users\97059\prooobject_22222.PWB			
		Case Totals (for in-service devices only)	
		MW	Mvar
		Load	250.0
		Generation	250.7
		Shunts	0.0
		Losses	0.7
		Dist Gen	0.0
		Generator Spinning Reserves	
		Positive [MW]	Negative [MW]
		1749.3	250.7
		Negative MW Loads and Generators	
		MW	Mvar
		Load	0.0
		Generation	0.0
		Slack Buses:	
		Bus 1 (1); in Area 1 (1)	
Print		Help Close	

Figure 24: total load when shunt =28Mvar

Adding a capacitor reduces the loaded reactive power which helps to reduce the voltage drop in the transmission line by lowering losses and improving efficiency the capacitor enhanced voltage stability, reduced losses, and improved system performance since the value of Mvar increases in the bus the total reactive power in the network decreases before adding the shunt the value of the reactive power in line two was -58.74Mvar after adding the capacitor it decreases to -43.82Mvar it also help to make the system more stable the required shunt capacitance to make the voltage in bus 4 equal 1 pu is 38Mvar and if the value of the shunt capacitance increases the losses of the system will decrease and the system becomes more stable

Question 5 Fault

to calculate the parameter z_o in pu

$$Z_{OPU} = \frac{Z_o \text{ Actual}}{Z_{base}} = \frac{0.2 + j1.5}{529} * 18 = 0.01058 + j0.079338$$

Branch Options dialog for Transmission 1 line fault parameter. Line 2, From Bus 2, To Bus 3, Circuit 1. Parameters: R=0.005671, X=0.042571, C=0.000000. Ground Impedance: R=0.000000, X=0.000000. Secondary Zero Sequence Imp: R2=0.000000, X2=0.000000. Neutral Impedance: Neutral R=0.000000, Neutral X=0.000000.

Branch Options dialog for Transmission 2 line fault parameter. Line 4, From Bus 4, To Bus 3, Circuit 1. Parameters: R=0.010580, X=0.079338, C=0.000000. Ground Impedance: R=0.000000, X=0.000000. Secondary Zero Sequence Imp: R2=0.000000, X2=0.000000. Neutral Impedance: Neutral R=0.000000, Neutral X=0.000000.

Branch Options dialog for Transmission 3 line fault parameter. Line 4, From Bus 4, To Bus 5, Circuit 1. Parameters: R=0.151230, X=0.113420, C=0.000000. Ground Impedance: R=0.000000, X=0.000000. Secondary Zero Sequence Imp: R2=0.000000, X2=0.000000. Neutral Impedance: Neutral R=0.000000, Neutral X=0.000000.

Figure 29: Transmission 1 line fault parameter

Figure 28: Transmission 2 line fault parameter

Figure 27: Transmission 3 line fault parameter

Branch Options dialog for Transmission 4 line fault parameter. Line 6, From Bus 5, To Bus 5, Circuit 1. Parameters: R=0.056711, X=0.042532, C=0.000000. Ground Impedance: R=0.000000, X=0.000000. Secondary Zero Sequence Imp: R2=0.000000, X2=0.000000. Neutral Impedance: Neutral R=0.000000, Neutral X=0.000000.

Branch Options dialog for Transmission 5 line fault parameter. Line 4, From Bus 4, To Bus 6, Circuit 1. Parameters: R=0.189036, X=0.141675, C=0.000000. Ground Impedance: R=0.000000, X=0.000000. Secondary Zero Sequence Imp: R2=0.000000, X2=0.000000. Neutral Impedance: Neutral R=0.000000, Neutral X=0.000000.

Figure 26: Transmission 4 line fault parameter

Figure 25: Transmission 5 line fault parameter

Figure 32:pv generator fault settings

Figure 31:slack generators fault parameter

Run Faults Abort

Single Fault

Calculate Clear Clear/Close

Choose the Faulted Bus

Sort by: ☒ Name ☐ Number

Bus	Name	Voltage (kV)
Bus 2 (2)	Bus 2	230.0 kV
Bus 3 (3)	Bus 3	230.0 kV
Bus 1 (1)	Bus 1	13.80 kV
Bus 4 (4)	Bus 4	230.0 kV
Bus 5 (5)	Bus 5	230.0 kV
Bus 6 (6)	Bus 6	230.0 kV
Bus 7 (7)	Bus 7	15.00 kV

Bus Records Lines Generators Loads Switched Shunt Buses Y-Bus Matrices

Number	Name	Phase Volt A	Phase Volt B	Phase Volt C	Phase Ang A	Phase Ang B	Phase Ang C
1	Bus1	0.60784	0.60784	0.60784	2.99	-117.01	122.99
2	Bus 2	0.16372	0.16372	0.16372	-5.13	-125.13	114.87
3	Bus 3	0.10625	0.10625	0.10625	-5.38	-125.38	114.62
4	Bus4	0.00000	0.00000	0.00000	-178.15	61.85	-58.15
5	Bus5	0.07947	0.07947	0.07947	10.16	-109.82	130.16
6	Bus6	0.10969	0.10969	0.10969	10.47	-109.53	130.47
7	Bus7	0.55200	0.55200	0.55200	18.60	-101.40	138.60

Fault Location: ☒ Bus Fault ☐ In-Line Fault
 Fault Type: ☐ Single Line-to-Ground ☒ 3 Phase Balanced ☐ Double Line-to-Ground
 Location %: 0
 Fault Impedance: R: 0.00000 X: 0.00000
 Fault Current: Scale Current By: 1.00000
 IF Magnitude: 8.257 p.u.
 IF Scaled Mag: 8.257 p.u.
 IF Angle: -78.06 deg.
 Units: ☒ p.u. ☐ Ampe
 Subtransient Phase Current: A 8.257 -78.06 deg. B 8.257 161.94 C 8.257 41.94

Figure 33:bus record while the fault

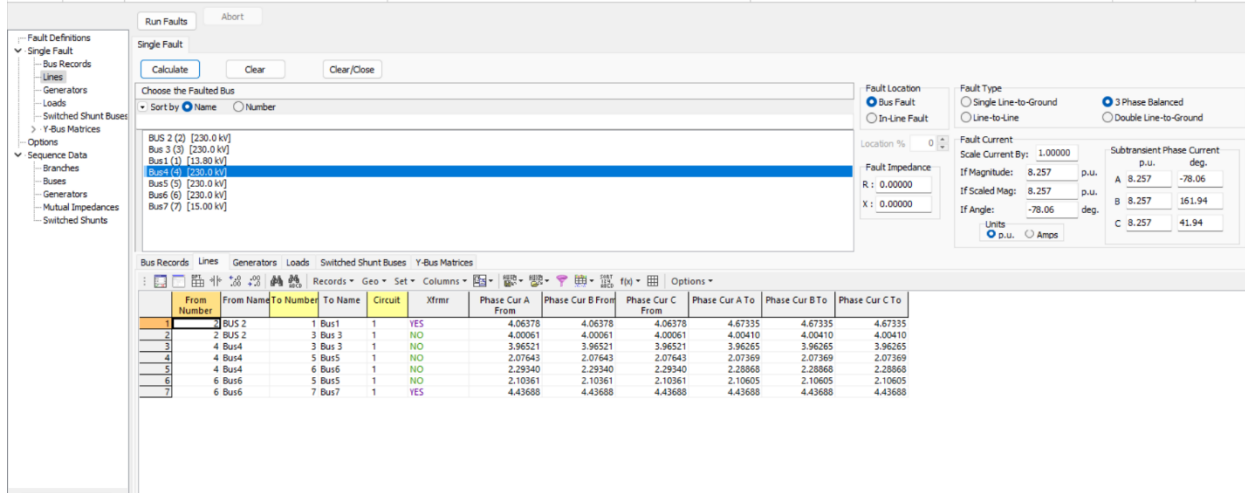


Figure 34: lines recorded

A three-phase balanced fault is applied to multiple buses in the system, resulting in the highest fault current magnitude at bus 4 where the voltage at it becomes 0 and the current 8.257 with angle -78.06 this test helps to take the worst case that can happen to the system and take the necessary transmission line cable and protection that should be used to avoid the current born

Conclusion

The knowledge of the power word simulator was taken, where the system was built, designed, and analyzed using the power word, the Y Bus matrix, power flow, losses, and voltages on buses were determined, and the T1 was set to be fully loaded, and the value of the load that makes it full loaded 150MW and a shunt capacitor was added to bus 4 to see the effect of the shunt capacitance, where it helps the system to be more stable and reduces the losses, a three-phase fault was made on bus 4 and the value of current was determined and the results of the fault on the system was seen and analyzed